

# LOGIC GATES

Nkechi Grace Okoacha

November 21, 2021

## Contents

1	logic gates	3
2	TYPES OF LOGIC GATES	3
3	AND GATE	4
4	OR GATE	4
5	NOT GATE	4
6	NOR	6
7	NAND	8
8	SUMMARY	11
9	QUIZ	13

# 1 logic gates

A logic gate is a building block of a digital circuit which is at the heart of any computer operation.

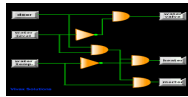


Figure 1: logic gates

Behind every digital system is a logic gate

Logic gates perform logical operations that take binary input (0s and 1s) and produce a single binary output. They are used in most electronic device including



(a) coffee



(b) Memory de-  
vices



(c) smartphone

## 2 TYPES OF LOGIC GATES

Now think of a logic gate like a light switch, it is either in an ON or OFF position. Similarly, the input output terminals are always in one of two binary positions false(0) and true(1). Each gate has its own logic or set of rules that determines how it acts based on multiple inputs outlined in a truth table.

Combining 10s, 1000s or millions of logic gates makes it possible for a computer to perform highly complex operations and tasks at ever increasing speeds.

A gate is a basic electronic circuit which operates on one or more signals to produce an output signal. Logic gates are digital circuits constructed from diodes, transistors, and resistors connected in such a way that the circuit output is the result of a basic logic operation (OR, AND, NOT) performed on the inputs.

Fundamental gates are AND, OR and NOT

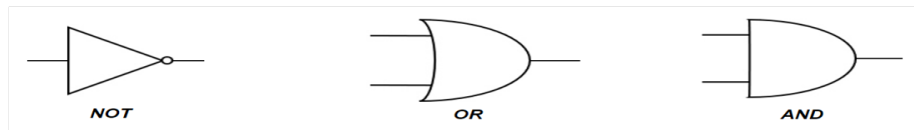


Figure 3: not, or, and gate

Derived Gates are NAND, NOR, XOR and XNOR (derived from the fundamental gates)

Universal Gates are NAND and NOR gates (the fundamental logic gates can be realized through them).

### 3 AND GATE

The expression  $C = A \times B$  reads as “C equals A AND B”. The multiplication sign (X) stands for the AND operation, same for ordinary multiplication of 1s and 0s.



Az	B	C=A X B
1	1	1
1	0	0
0	1	0
0	0	0

### 4 OR GATE

The expression  $C = A + B$  reads as “C equals A OR B”. It is the inclusive “OR”. The Addition (+) sign stands for the OR operation

### 5 NOT GATE

The NOT gate is called a logical inverter

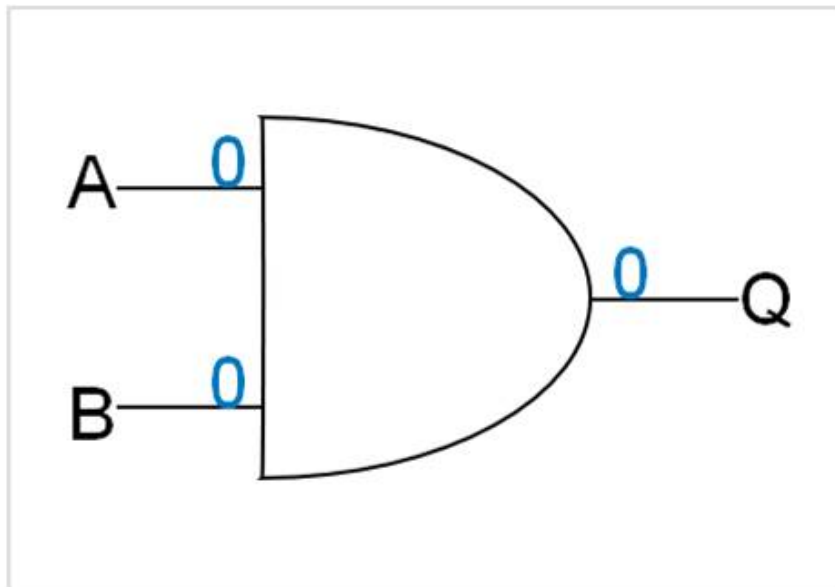


Figure 4: AND GATE


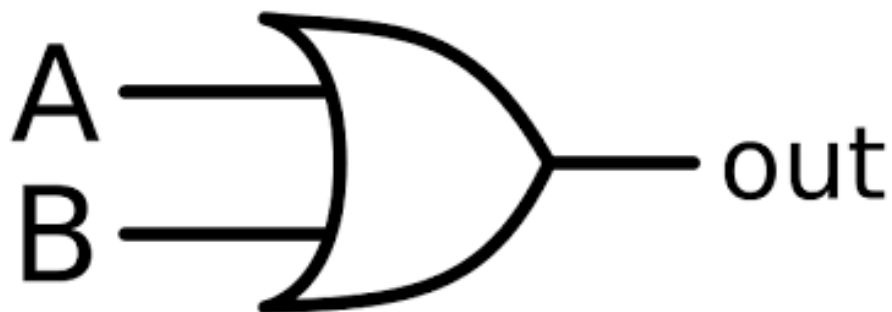


Figure 5: or gate

A	B	C=A + B
1	1	1
1	0	1
0	1	1
0	0	0

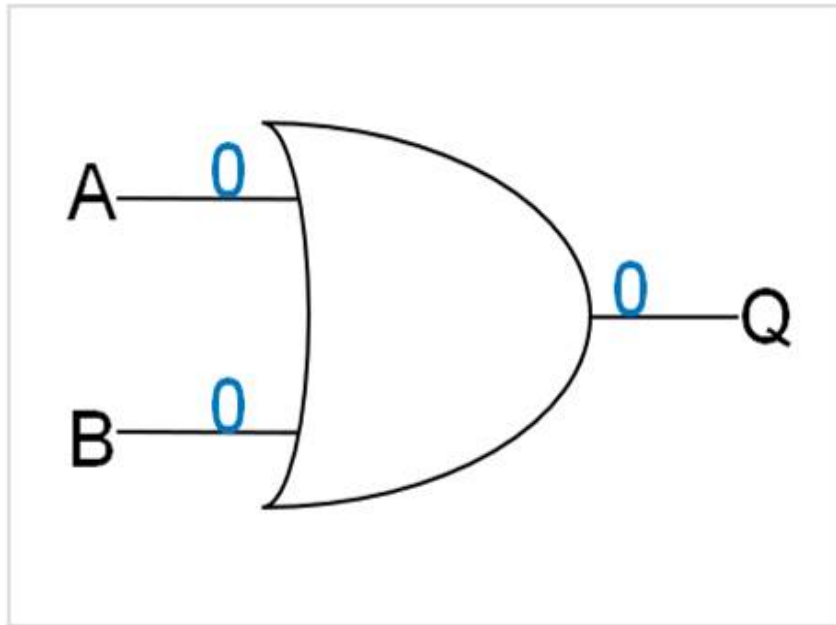- It has only one input. It reverses the original input (A) to give an inverted output C
- $C = \text{NOT } A$  or  $C = \overline{A}$



- The NOR (NOT OR) gate circuit is an inverter OR gate



$$C = \overline{(A + B)}$$

- Reads as C = NOT of A or B
- The NOR Gate gives a true output (result of 1) only when both inputs are false (0)

The NOR Gate is a universal gate because it can be used to form any other kind of gate


Figure 6: nor gate

## 6 NOR

The NOR (NOT OR) gate circuit is an inverter OR gate

$$c = \overline{(A + B)}$$

A	C = $\bar{A}$
1	0
0	1

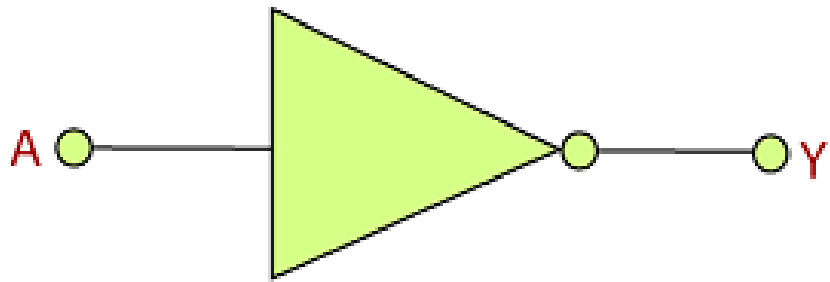

## NOT Gate

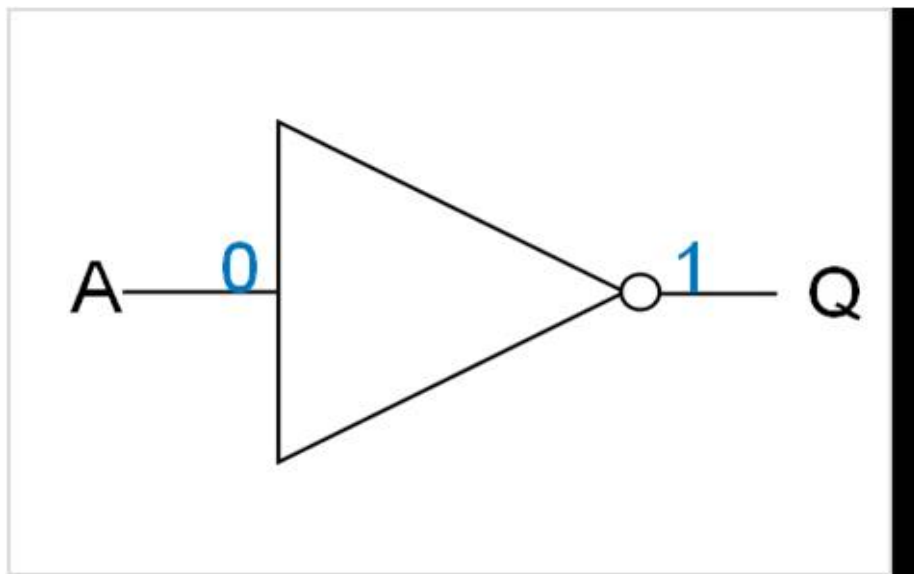


Figure 7: not gate

Reads as  $C = \text{NOT of } A \text{ or } B$  The NOR Gate gives a true output (result of 1) only when both inputs are false (0)

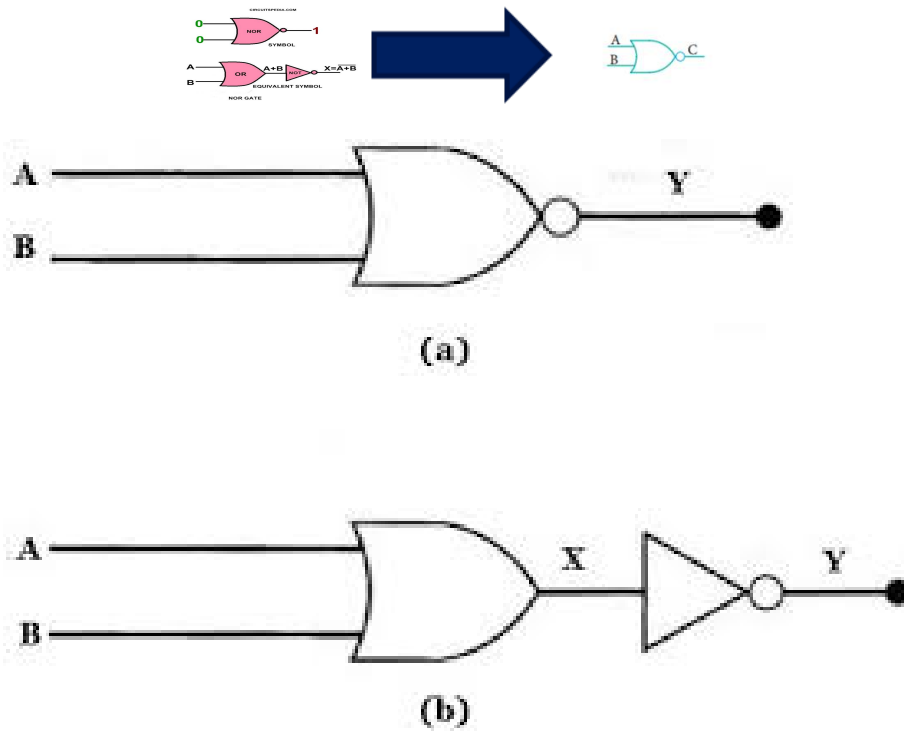


Figure 9: nor gate

A	B	$C = A + B$	$C \overline{A + B}$
1	1	1	0
1	0	1	0
0	1	1	0
0	0	0	1

## 7 NAND

The NAND (NOT AND) Gate is an inverted AND gate

$$C = \overline{A \cdot B}$$

The NAND Gate gives a false output (result of 0) only when both inputs are true (1)

- An XOR (exclusive OR) gate acts in the same way as the exclusive OR logical connector.
- It gives a true output (result of 1) if one, and only one, of the inputs to the gate is true (1), i.e. either or but not both




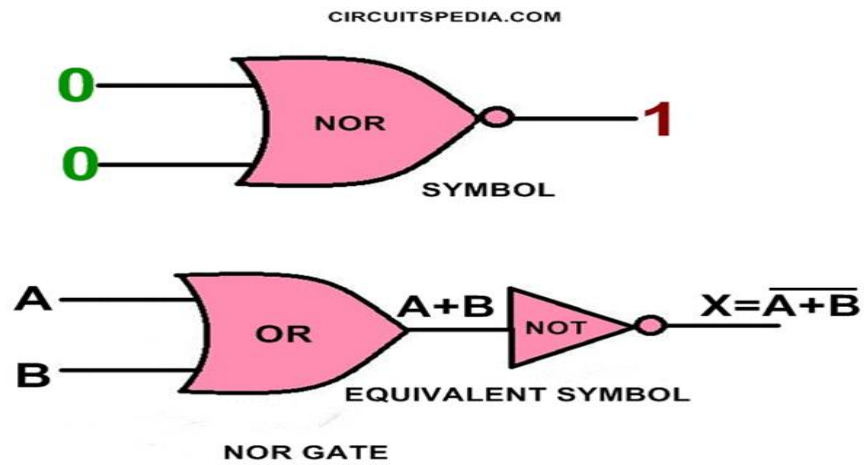



Figure 10: nor gate

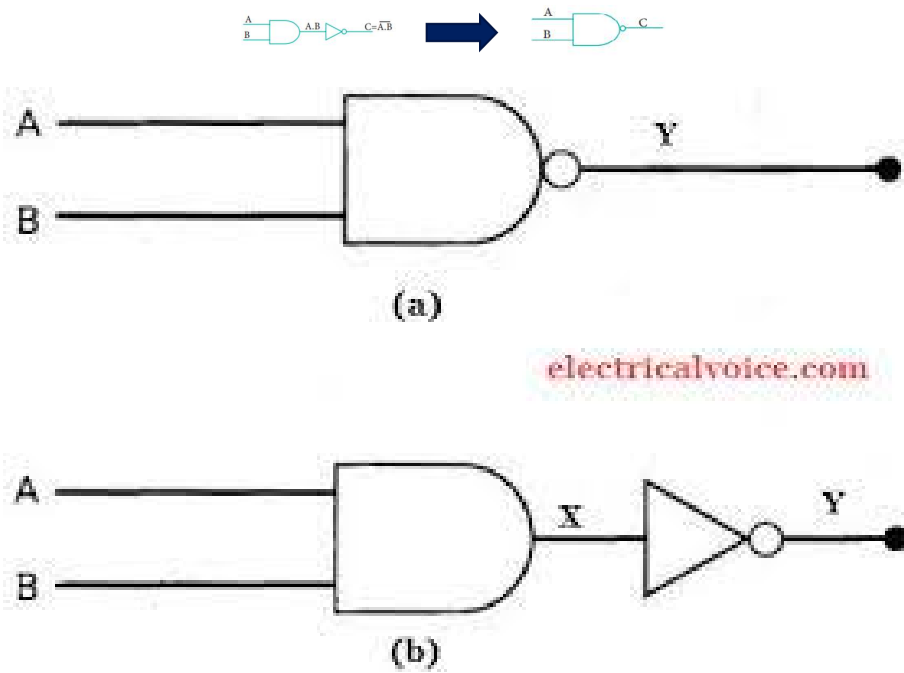

captionnand


- $C = \overline{A} + B = \overline{A}.B + \overline{B}.A$
- The XNOR (exclusive-NOR) gate is a combination XOR gate followed by

A	B	A x B	$C = \overline{A \times B}$
1	1	1	0
1	0	0	1
0	1	0	1
0	0	0	1

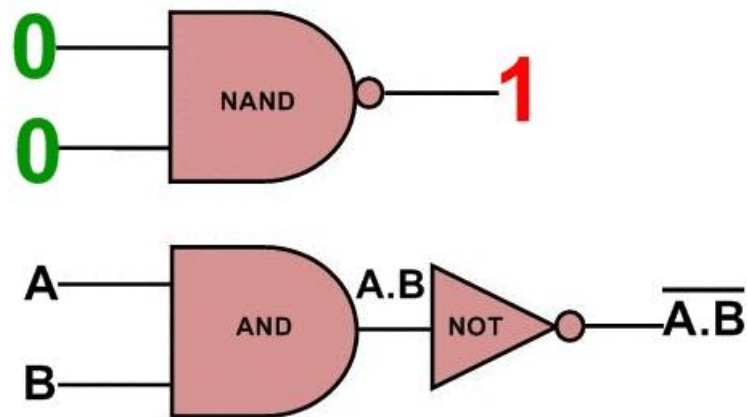

## NAND gate

Figure 12: nand gate

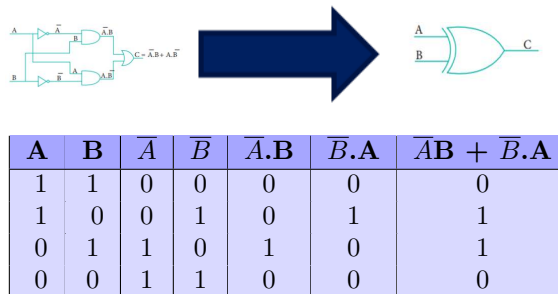

A	B	$\bar{A}$	$\bar{B}$	$\bar{A}.B$	$\bar{B}.A$	$\bar{A}B + \bar{B}.A$
1	1	0	0	0	0	0
1	0	0	1	0	1	1
0	1	1	0	1	0	1
0	0	1	1	0	0	0

an inverter. It is represented by the

- Its gives a true output(1),if the inputs are different.

$$C = A + B = \bar{A}.B + \bar{B}.A$$

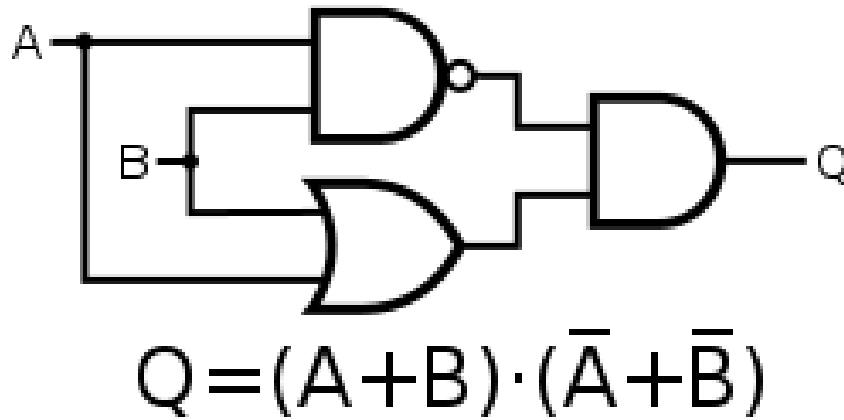


Figure 14: XOR gate

A	B	$\bar{A}$	$\bar{B}$	$A \cdot B$	$\bar{B} \cdot A$	$\bar{A}B + \bar{B}A$	$\bar{A}B + \bar{B}A$
1	1	0	0	0	0	0	1
1	0	0	1	0	1	1	0
0	1	1	0	1	0	1	0
0	0	1	1	0	0	0	1

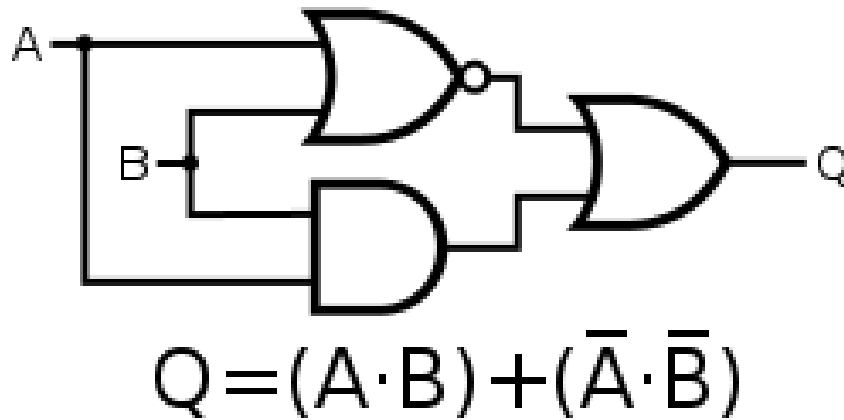


Figure 16: XNOR gate

## 8 SUMMARY

- Using different combination of logic gates, complex operations can be performed.








Logical Gates	Symbol	Truth Table															
AND		<table><tr><th>A</th><th>B</th><th>AB</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	AB	0	0	0	0	1	0	1	0	0	1	1	1
A	B	AB															
0	0	0															
0	1	0															
1	0	0															
1	1	1															
OR		<table><tr><th>A</th><th>B</th><th>A + B</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	A + B	0	0	0	0	1	1	1	0	1	1	1	1
A	B	A + B															
0	0	0															
0	1	1															
1	0	1															
1	1	1															
NOT		<table><tr><th>A</th><th><math>\overline{A}</math></th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	A	$\overline{A}$	0	1	1	0									
A	$\overline{A}$																
0	1																
1	0																
NAND		<table><tr><th>A</th><th>B</th><th><math>\overline{AB}</math></th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	$\overline{AB}$	0	0	1	0	1	1	1	0	1	1	1	0
A	B	$\overline{AB}$															
0	0	1															
0	1	1															
1	0	1															
1	1	0															
NOR		<table><tr><th>A</th><th>B</th><th><math>\overline{A + B}</math></th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	$\overline{A + B}$	0	0	1	0	1	0	1	0	0	1	1	0
A	B	$\overline{A + B}$															
0	0	1															
0	1	0															
1	0	0															
1	1	0															
XOR		<table><tr><th>A</th><th>B</th><th><math>A \oplus B</math></th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	$A \oplus B$	0	0	0	0	1	1	1	0	1	1	1	0
A	B	$A \oplus B$															
0	0	0															
0	1	1															
1	0	1															
1	1	0															
XNOR		<table><tr><th>A</th><th>B</th><th><math>\overline{A \oplus B}</math></th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	$\overline{A \oplus B}$	0	0	1	0	1	0	1	0	0	1	1	1
A	B	$\overline{A \oplus B}$															
0	0	1															
0	1	0															
1	0	0															
1	1	1															


Figure 17: LOGIC GATES AND THEIR TRUTH TABLES

- With the Universal logic gates - NAND and NOR, any other gate can be built
- There is no limit to the number of gates that can be arranged together in a single device.
- However, in practice, there is a limit to the number of gates that can be packed into a given physical space.
- Arrays of logic gates are found in digital integrated circuits.
- The logic gates are abstract representations of real electronic circuits
- In computers, Logic gates are built using transistors combined with other electrical components like resistors and diodes.

- These electrical components are wired together in order to transform a particular input to give a desired output
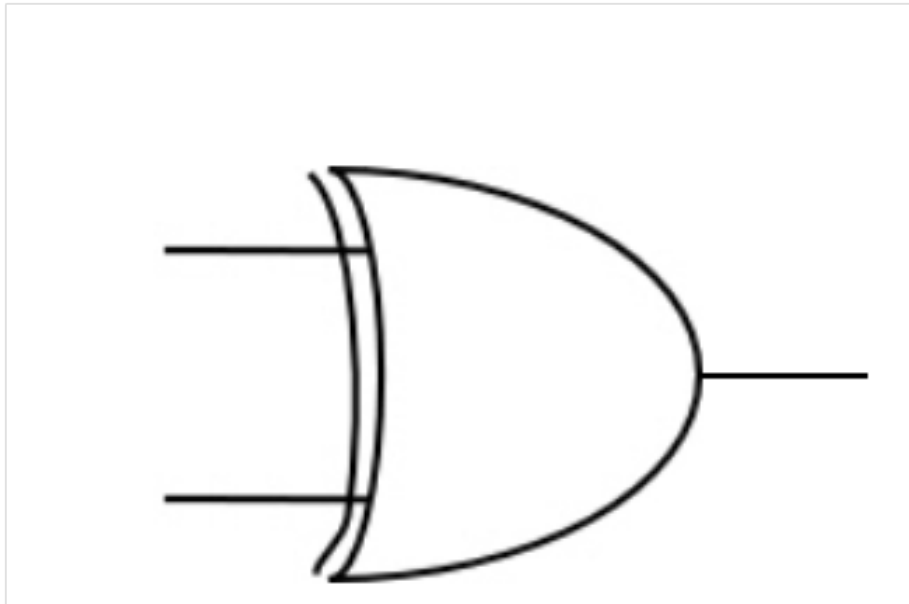
## 9 QUIZ

- What is the output of an AND gate if the inputs are 1 and 0?
- Explain the difference between the AND gate and the OR gate.
- What is the output of a NOT gate if the inputs is 0?
- Which logic gate is this?
- Which gate is also known a logical converter?



Thank  
you!